

EXP No: 2GATES USING IC

Aim: Verify the logic behavior of various IC gates 7408, 7432, 7404, 7400.

Objectives: \* to study the working of logic gates, (OR, AND, NOT, NOR, NAND, XOR) using IC and verify truth tables.

Components: Bread board, kit, 7408, 7432, 7404, 7400, 7402, 7486

Theory

a) An OR gate is a logic circuit with 2 or more inputs and one output. The output of an OR is low <sup>only</sup> when all of its inputs are low for all other possible input combinations the output is high.

b) The output of an AND gate is high only when all of its inputs are in the high state. In all other cases the output is low.

c) A NOT gate is a one input/one output logic circuit whose output is always the complement of the input. That is a low input produces high output and vice versa.

d) The output of a NOR gate is a logic '1' when all its inputs are logic '0' for all other input combinations the output is logic '0'.

e) The output of a NAND Gate is a logic '0' when all its inputs are logic '1' for all other input combinations the output is a logic '1'.

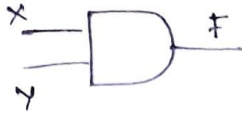
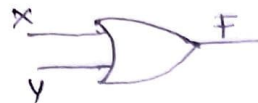

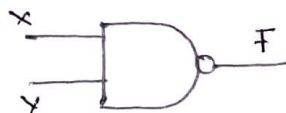
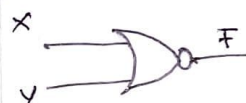

### Procedure

- a) Test all the IC's manually with IC tester
- b) Connect VCC and the ground
- c) Connect the appropriate pins to the input and output LED's and switches.
- d) verify the truth table with respect to the clock.

### Result

Different logic gates and their truth table are verified.

# \* CIRCUITS AND TRUTH TABLES

| Name   | Graphic symbol  | Algebraic function           | Truth table  |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |
|--------|---|------------------------------|--|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|
| * AND  |    | $F = x \cdot y$              | <table><tr><th>x</th><th>y</th><th>F</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table> | x | y | F | 0 | 0 | 0 | 0 | 1 | 0 | 1 | 0 | 0 | 1 | 1 | 1 |
| x      | y   | F                            |  |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |
| 0      | 0   | 0                            |  |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |
| 0      | 1   | 0                            |  |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |
| 1      | 0   | 0                            |  |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |
| 1      | 1   | 1                            |  |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |
| * OR   |    | $F = x + y$                  | <table><tr><th>x</th><th>y</th><th>F</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table> | x | y | F | 0 | 0 | 0 | 0 | 1 | 1 | 1 | 0 | 1 | 1 | 1 | 1 |
| x      | y   | F                            |  |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |
| 0      | 0   | 0                            |  |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |
| 0      | 1   | 1                            |  |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |
| 1      | 0   | 1                            |  |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |
| 1      | 1   | 1                            |  |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |
| * NOT  |  | $F = x'$                     | <table><tr><th>x</th><th>F</th></tr><tr><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td></tr></table>   | x | F | 0 | 1 | 1 | 0 |   |   |   |   |   |   |   |   |   |
| x      | F   |                              |  |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |
| 0      | 1   |                              |  |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |
| 1      | 0   |                              |  |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |
| * NAND |  | $F = (x \cdot y)'$           | <table><tr><th>x</th><th>y</th><th>F</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table> | x | y | F | 0 | 0 | 1 | 0 | 1 | 0 | 1 | 0 | 0 | 1 | 1 | 0 |
| x      | y   | F                            |  |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |
| 0      | 0   | 1                            |  |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |
| 0      | 1   | 0                            |  |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |
| 1      | 0   | 0                            |  |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |
| 1      | 1   | 0                            |  |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |
| * NOR  |  | $F = (x + y)'$               | <table><tr><th>x</th><th>y</th><th>F</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table> | x | y | F | 0 | 0 | 1 | 0 | 1 | 0 | 1 | 0 | 0 | 1 | 1 | 0 |
| x      | y   | F                            |  |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |
| 0      | 0   | 1                            |  |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |
| 0      | 1   | 0                            |  |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |
| 1      | 0   | 0                            |  |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |
| 1      | 1   | 0                            |  |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |
| * XOR  |  | $F = xy' + x'y$<br>$= x + y$ | <table><tr><th>x</th><th>y</th><th>F</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table> | x | y | F | 0 | 0 | 0 | 0 | 1 | 1 | 1 | 0 | 1 | 1 | 1 | 0 |
| x      | y   | F                            |  |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |
| 0      | 0   | 0                            |  |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |
| 0      | 1   | 1                            |  |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |
| 1      | 0   | 1                            |  |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |
| 1      | 1   | 0                            |  |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |