

DEMONSTRATION OF UNIVERSAL GATESREALIZATION OF BASIC GATES USING NAND GATES

Aim: To implement AND, OR, NOT gates using NAND gates.

Objectives: To study the design and implementation of logic gates using universal gates.

Components: Bread board / kit, 7400, 7402

Theory.

- a) An OR gate is a logic circuit with 2 or more inputs and one output. The output of an OR gate is low only when all of its inputs are low. For all other possible input combinations the output is high.
- b) The output of an AND gate is high only when all of its inputs are in high state. In all other cases, the output is low.
- c) A NOT gate is a one-output/one-input gate, whose output is always the complement of the input. That is, a low input produces a high output & vice versa.
- d) The output of a NOR gate is a logical '1' when all its inputs are logic '0'. For all other input combinations the output is logic '0'.
- e) The output of a NAND gate is a logic '0' when all its inputs are a logic '1'. For all input combinations the output is a logic '1'.

### Procedure

- a) test all the ICs manually / using IC tester
- b) connect VCC and the ground
- c) connect the appropriate pins at the input & output LEDs and switches.
- d) verify the truth table with respect to the clock.


### Result

Different logic gates are constructed and their truth tables are verified.



## CIRCUIT DIAGRAMS

Realization of gates using NAND

NOT gate

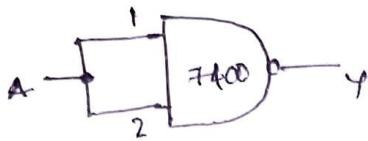

AND GATE

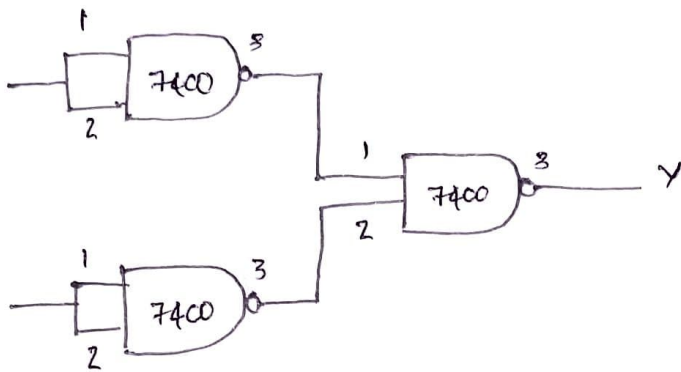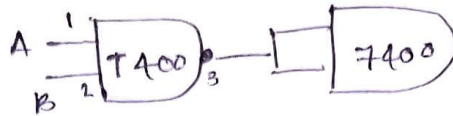

NOT gate circuits

