

Realisation of Gates using NOR

Name: Demonstration of Universal gates.

Aim: Implement logic gates using universal gate NOR

Objective: To study the design and implementation of logic gates (OR, AND, NOT, NOR, NAND, XOR) using universal gates (NAND, NOR) & verify their truth table.

Components: Bread board / kit, 7400, 7402.

Theory:

- An OR gate is a logic circuit with 2 or more inputs and one output. The output of an OR is low when all of its inputs are low for all other possible input combinations the output is high.
- The output of an AND gate is high only when all of its inputs are in the high state <sup>in</sup> all other situations the output is low.
- A NOT gate is a one-input/one-output logic circuit whose output is always the complement of the input, that is a low input produces high output and vice versa.
- The output of a NOR gate is a logic '1' when all its inputs are logic '0' for all other input combinations the output is logic '0'.
- The output of a NAND gate is a logic '0' when all its inputs are logic '1' for all other inputs combinations the output is a logic '1'.

### Procedure

- a) test all the IC's manually / using IC tester
- b) connect VCC and the ground
- c) connect the appropriate pins at the input & output LEDs and switches
- d) verify the truth table with respect to the clock

### Result

Different logic gates are constructed and their truth tables are verified.

## Realization of gates using NOR

