

Experiment NO: 11

Name: S-R Latch using NAND.

Aim: Construct, test and investigate the operation of SR latch using NAND.

Objectives: To study the construction and the working of SR latch using NAND.

Components: Bread board/ kit, 7400

Theory:

SR-latch: The SR latch is a circuit with two cross-coupled NOR gates or two cross-coupled NAND gates, and two inputs labelled S for SET and R for RESET. The SR latch has 2 useful states. $Q=1$ and $Q'=0$ the latch is said to be in SET state.

When $Q=0$ and $Q'=1$ the latch is said to be in RESET state.

Outputs Q and Q' are normally the complemented of each other. However, when both inputs are equal to 1 at the same time, a condition in which both outputs are equal to '0' occurs.

If both inputs are then switched to 0 simultaneously the device will enter an unpredictable or undefined state or a metastable state.


Procedure

1. Connections are made as per the circuit diagram.
2. Switch on the power supply.
3. Apply different combinations of inputs and observe the output, compare the output with the truth tables.

Result

Different logic circuits are constructed & truth tables verified.

Circuit diagram

 

Truth table

S	R	Q	Q'	
1	0	0	1	
1	1	0	1	(after $S=1, R=0$)
0	1	1	0	
1	1	1	0	(after $S=0, R=1$)
0	0	1	1	(Forbidden)